

# Review of Digital Design Fundamentals

---

- 
- **Bit:** A *binary* digit; can have a value of 0 or 1
  
  - **Logic gate:** A digital circuit that manipulates bits. A logic gate takes one or more bits as input(s) and generates one bit as the output.
    - A logic gate can be represented pictorially by its logic symbol. The function performed by a logic gate can also be expressed *algebraically*, or in terms of a *Truth Table*.
  
  - **Logic diagram:** A diagram showing an interconnection of logic symbols.



## Truth table

---

- ❑ **Truth table:** The truth table gives the input-output relation of a logic gate or logic circuit in tabular form.
- ❑ It specifies the output bit(s) for each possible input bit combination.
- ❑ A circuit with  $n$  binary inputs has  $2^n$  different input combinations.
- ❑ A binary value of 0 is sometimes referred to as L (low) or F (false).
- ❑ A binary value of 1 is sometimes referred to as H (high) or T (true).



## Minterm


---

- **Minterm:** One specific combination of input bits, out of the  $2^n$  different input combinations.
- A truth table of  $n$  binary inputs has  $2^n$  minterms and an output is specified for each minterm.

# Logic Gates


---

Logic Symbols:

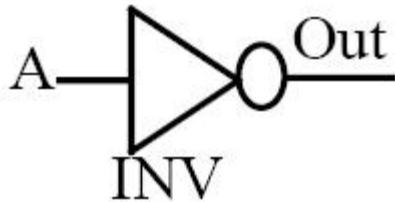

A	out
0	1
1	0

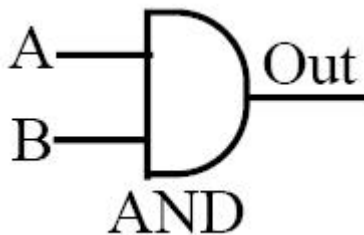$\overline{A}$ ,  $\sim A$ ,  $A'$ ,  $\neg A$




A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

$A \cdot B$ ,  $AB$ ,  $A*B$ ,  $A \wedge B$

# Logic Gates

---

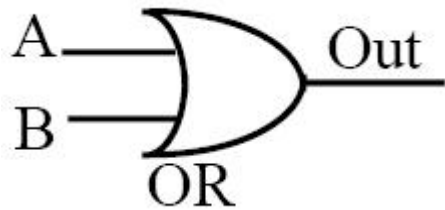

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


$$A+B, A \vee B$$



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0


$$A \oplus B$$

# Logic Gates

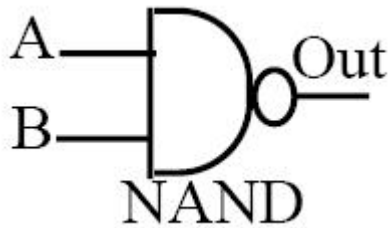

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0
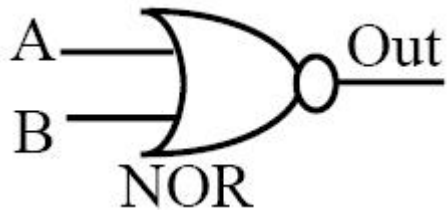
$$\overline{AB}, \overline{A.B}, \overline{A*B}, (A \wedge B)'$$



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$$\overline{A+B}, (A \vee B)'$$

# Logic Gates

---



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{A \oplus B}$$




# Digital Circuit Representation

---

- The truth table, logic diagram and algebraic expression are three different ways of representing a digital circuit and given one form the other representations of the circuit can be derived.
- The truth table representation of a Boolean function is unique, but the same function may have more than one logic or algebraic representation.
- EXAMPLE: Given the following logic diagram, obtain the corresponding truth table and algebraic expression.

## Digital Circuit Representation

---

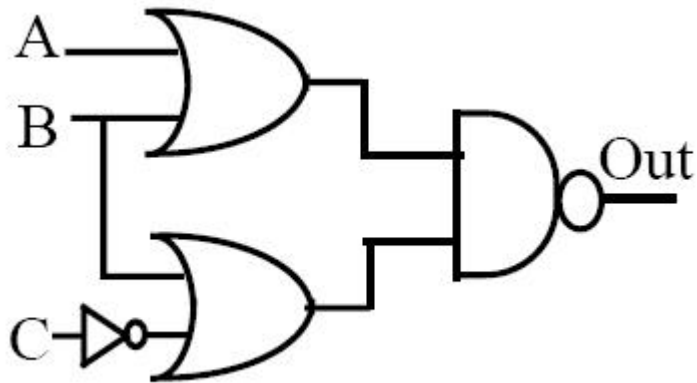

$$\text{Out} = \overline{(A+B)(B+\overline{C})}$$

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

## Basic Identities of Boolean algebra

---

$x + 0 = x$	$x \cdot 0 = 0$
$x + 1 = 1$	$x \cdot 1 = x$
$x + x = x$	$x \cdot x = x$
$x + x' = 1$	$x \cdot x' = 0$
$x + y = y + x$	$x \cdot y = y \cdot x$
$x + (y + z) = (x + y) + z$	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$
$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
$(x + y)' = x' \cdot y'$	$(x \cdot y)' = x' + y'$
$(x')' = x$	



## K-Map

---

- ❑ The complexity of a digital circuit depends on the complexity of the corresponding algebraic expression.
- ❑ The karnaugh map (k-map) provides a simple straightforward procedure for simplifying Boolean expressions and thereby obtaining simpler digital circuits.

## K-Map

---

- ❑ A diagram made up of squares, where each square represents a minterm.
- ❑ The output (0 or 1) for a specific minterm is inserted in the corresponding square in the k-map.
- ❑ A function with  $n$  variables has a kmap with  $2^n$  squares.

# Properties of k-maps

---

- Each row (or column) in the k-map is labelled by one or more bits, representing the values of the corresponding variables for that row (or column).
- The minterm corresponding to a particular square in the k-map (belonging to the  $i^{\text{th}}$  column and  $j^{\text{th}}$  row) is obtained by taking the values of the variables associated with the  $i^{\text{th}}$  column and  $j^{\text{th}}$  row.

		AB			
		00	01	11	10
C	0				
	1				

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				
	00				

For example the shaded squares in figure 1 (a) and (b) correspond to minterms 111 and 0110 respectively.



## Rules for simplifying k-maps

---

1. Plot a Boolean function on to a k-map by inserting 1's in those squares where the corresponding minterm has an output of 1.
2. Combine *adjacent* 1's into groups such that:
  - i) a group contains only 1's
  - ii) the number of squares in a group is a power of 2
  - iii) the group is not part of a single larger group



## Rules for simplifying k-maps

---

3. Keep choosing additional groups until all the 1's in the k-map are covered i.e. each 1 is part of at least one group. Choose the groups in such a way that the total number of groups needed to cover all the 1's is minimized.
4. Obtain an algebraic product term for each group.
5. Obtain the final solution by a logical OR of all the terms from step 4.


## Some definitions:

---


- ❑ Implicant: A group of  $2^k$  adjacent 1's in a k-map.
- ❑ Prime Implicant (PI): An implicant which is not completely covered by a single larger implicant.
- ❑ Essential Prime Implicant: A prime implicant where at least one minterm is not covered by any other prime implicant.

# Examples

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

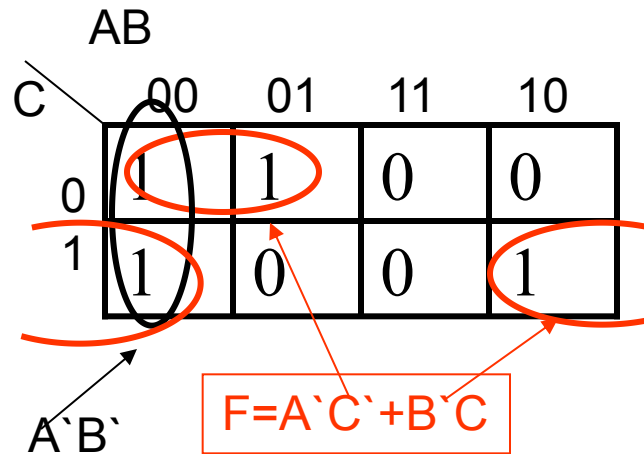


  
Essential PI

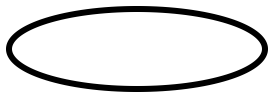  
Non-Essential PI

# Example

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

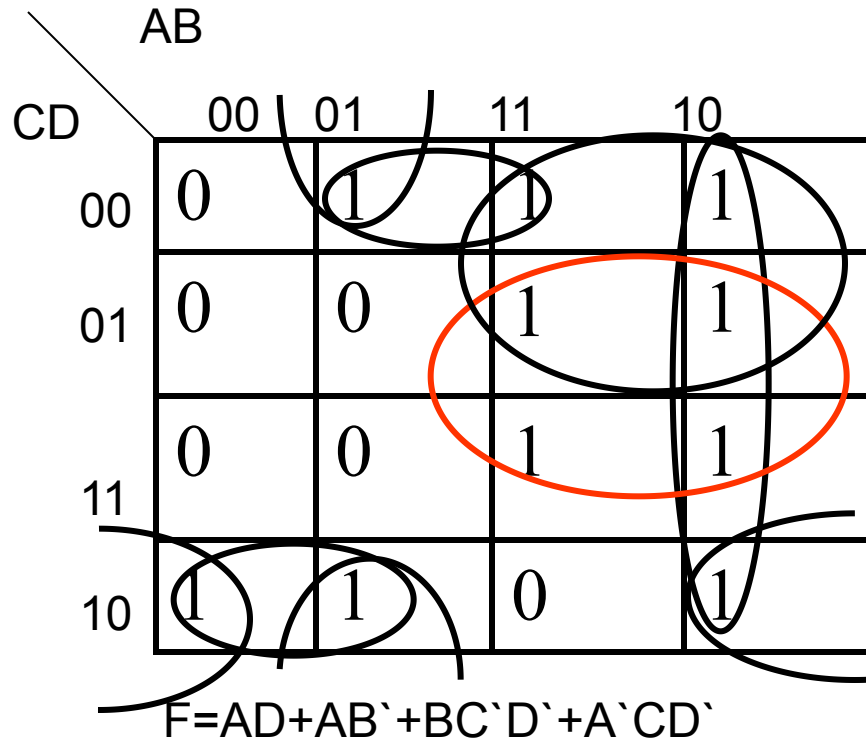

OR

$$F = AD + AC' + A'BD' + B'CD'$$



Non-Essential PI



Essential PI

# Don't Cares

---

- A truth table can be expressed in compact form by simply specifying the minterms for which the output is 1.
- For some functions, there may be certain input conditions for which we don't care what output is. This situation is represented by putting a "d" in the output for the corresponding minterms.
- Don't care outputs may be treated as either a 0 or a 1, in order to obtain a minimized circuit.
- All minterms which are not in the given list(s) are assumed to have an output of 0.

## Function with Don't cares

---

$$F(A,B,C) = \Sigma(0,2,6), d(A,B,C) = \Sigma(1,3,5)$$

- a) F has three inputs A,B, and C.
- b) The outputs corresponding to minterms 0,2,6 are 1.
- c) The outputs corresponding to minterms 1,3,5 are don't cares
- d) The outputs for all remaining minterms (4 and 7) are 0.

## Examples:

---

- Obtain a minimized SOP expression for the following functions. Also, list all the prime implicants and indicate which ones are essential.

$$(i) F(A,B,C) = \Sigma(0,2,6), d(A,B,C) = \Sigma(1,3,5).$$

Karnaugh map for  $F(A,B,C)$ :

		AB			
		00	01	11	10
C	0	1	1	1	0
	1	d	d	0	d

Groupings: A horizontal group of three 1s in row C=0 (minterms 0, 1, 2) and a vertical group of two 1s in column AB=00 (minterms 0, 1). Both groups are essential prime implicants.

Prime Implicants

$A'$ (essential)

$BC'$ (essential)

$$F = A' + BC'$$



(ii)  $F(A,B,C,D) = \Sigma(1,2,4,12)$ ,  $d(A,B,C,D) = \Sigma(3,5,9,11)$ .

		AB			
		00	01	11	10
CD	00	0	1	1	0
	01	1	d	0	d
	11	d	0	0	d
	10	1	0	0	0

$$F = B'D + BC'D' + A'B'C$$

### Prime Implicants

$BC'D'$ (Essential)

$A'B'C$ (Essential)

$B'D$

$A'BC'$

$A'C'D$

# Product of sums (POS)

---

- A POS expression for a function  $F$  can be obtained by grouping the 0,s in the k-map for  $F$  and then
  - (i) Obtain a SOP expression for  $F'$  and complement it OR
  - (ii) Directly obtain the POS expression by examining the selected groups.

(i)  $F(A,B,C,D) = \Sigma(0,2,4-6,8-10)$ ,  $d(A,B,C,D) = \Sigma(1,7)$ .

		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	d	1	0	1
	11	0	d	0	0
	10	1	1	0	1

Prime Implicants of  $F'$

AB (Essential)

CD(Essential)

$A'B'D$

$$F' = AB + CD$$

$$F'' = (AB + CD)'$$

$$F = (AB)' \cdot (CD)'$$

$$F = (A' + B') \cdot (C' + D')$$

Final POS expression

The same final expression can also be obtained by directly examining the groups.

$$(ii) F(A,B,C,D) = \Sigma(0-2,8-10,12-15).$$

		AB			
		00	01	11	10
CD	00	1	0	1	1
	01	1	0	1	1
	11	0	0	1	0
	10	1	0	1	1

Prime Implicants of F'

$A'B$  (Essential)

$B'CD$  (Essential)

$A'CD$

$$F' = A'B + B'CD$$

$$F'' = (A'B + B'CD)'$$

$$F = (A'B)' \cdot (B'CD)'$$

$$F = (A+B') \cdot (B+C'+D')$$

Final POS expression

The same final expression can also be obtained by directly examining the groups.

# Multi-output functions

---

- ❑ A multi-output function is treated similar to a single output function,
- ❑ A separate k-map and Boolean expression needs to be derived for each of the outputs.
- ❑ Example: full adder (FA) circuit which has 3 inputs - the 2 bits (A and B) to be added and a carry in ( $C_{in}$ ) and has 2 outputs a sum (S) and a carry out to the next stage ( $C_{out}$ ).

# Full Adder

A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A'B'C + A'BC' + AB'C' + ABC$$

$$S = A \oplus B \oplus C$$

$$C_{out} = AB + BC + AC$$

S AB

		00	01	11	10
C	0	0	1	0	1
	1	1	0	1	0

Cout AB

		00	01	11	10
C	0	0	0	1	0
	1	0	1	1	1



## flip-flops and Sequential Circuits

---

- ❑ **Combinational circuits**: Digital circuits where the output depends only on the current inputs. They consist of an interconnection of logic gates.
- ❑ **Sequential circuits**: Output depends on the previous output state as well as the current inputs.



# flip-flops and Sequential Circuits

---

- **Flip-Flops**: Basic storage element, capable of storing previous state (0 or 1). A flip-flop can store 1 bit of information and is the basic building block of sequential circuits.



# flip-flops and Sequential Circuits

---

- **Edge-triggered flip-flop**: State changes occur only during a positive (0 to 1) or negative (1 to 0) clock transition. The corresponding flip-flops are called *positive* or *negative* edge-triggered flip-flops respectively.

The output (*Next State*) of a flip-flop depends on


- Present State and
- Current inputs and is described in a characteristics table.

**Characteristic table**: Specifies the next state, based on present state and current inputs.

# SR-flip-flop

---


Input SR	Present State Q(t)	Next State Q(t+1)
00	0	0
00	1	1
01	0	0
01	1	0
10	0	1
10	1	1
11	Indeterminate	

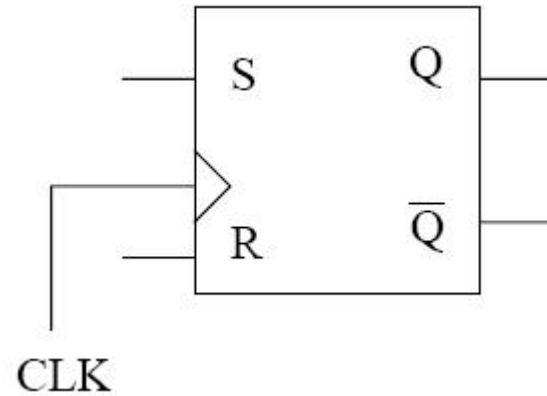

# JK-flip-flop


---

Input		Present	Next
S	R	State $Q(t)$	State $Q(t+1)$
00		0	0
00		1	1
01		0	0
01		1	0
10		0	1
10		1	1
11		0	1
11		1	0

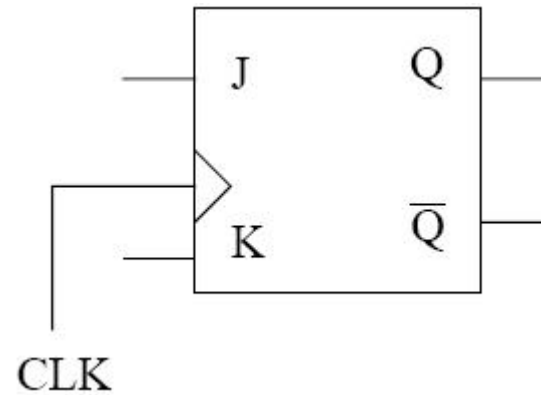

# D-flip-flop


Input D	Present State $Q(t)$	Next State $Q(t+1)$
0	0	0
0	1	0
1	0	1
1	1	1

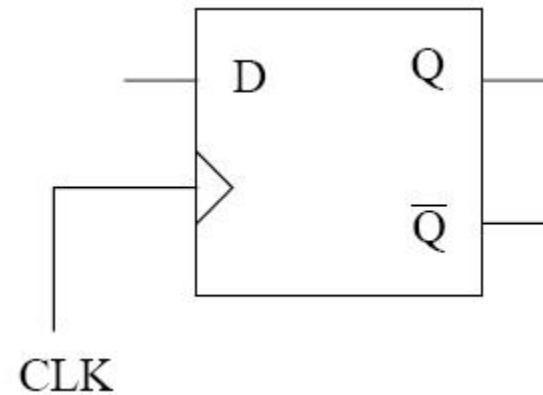

# T-flip-flop

---


Input T	Present State Q(t)	Next State Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

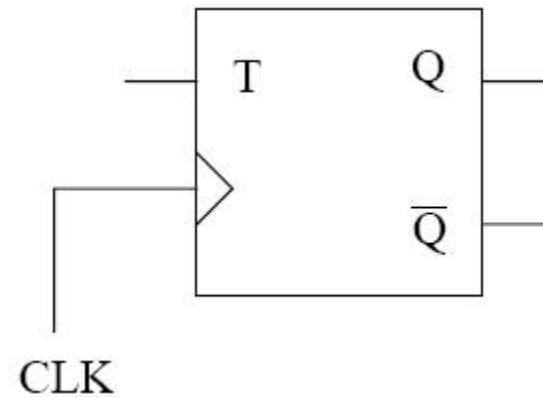

# Sequential Circuit Analysis

Complete the state table, for the following circuit.


present state input			flip-flop		next state	
A	B	X	inputs		A	B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	1	0
0	1	1	1	1	1	1
1	0	0	0	1	0	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

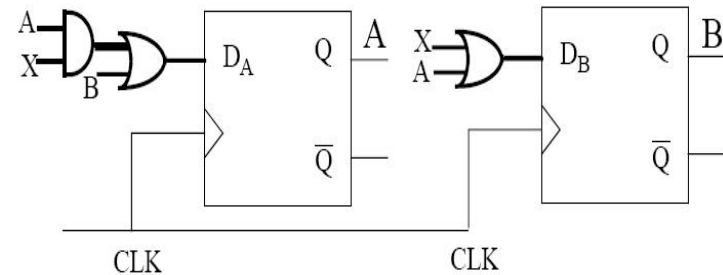

$$D_A = AX + B; D_B = X + A;$$

# Sequential Circuit Analysis

present state input			flip-flop inputs		next state	
A	B	X	$T_A$	$T_B$	A	B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	1	1
0	1	1	1	1	1	0
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	0	0
1	1	1	1	1	0	0

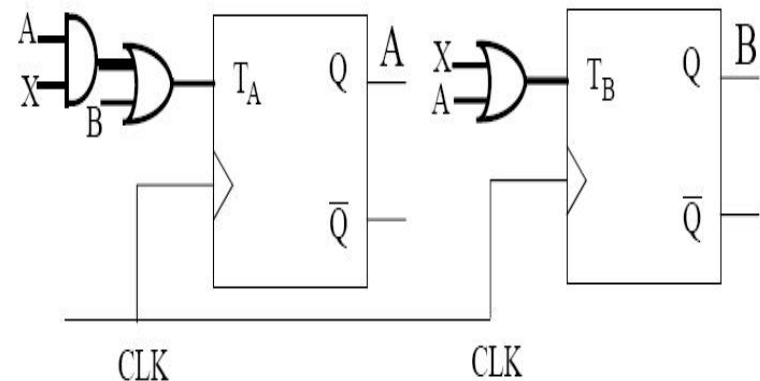

(ii) Complete the state table If T-flip-flops are used.

.  $T_A = AX + B$ ;  $T_B = X + A$ ;

## SR-flip-flop

## JK-flip-flop

---

### Excitation Tables

Present State Q(t)	Next state Q(t+1)	Inputs	
		S	R
0	0	0	d
0	1	1	0
1	0	0	1
1	1	d	0

Present State Q(t)	Next state Q(t+1)	Inputs	
		J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0



## D-flip-flop

## T-flip-flop

---

### Excitation Tables

Present State $Q(t)$	Next state $Q(t+1)$	Inputs $D$
0	0	0
0	1	1
1	0	0
1	1	1

Present State $Q(t)$	Next state $Q(t+1)$	Inputs $T$
0	0	0
0	1	1
1	0	1
1	1	0


# Sequential Circuit Design

---

- The excitation tables give the required inputs to the flip-flop for a specific change of state. The steps to be followed in the design of sequential circuits are as follows:
  1. Draw the state diagram from the problem specification
  2. Choose the type of flip-flop to be used.
  3. Fill in the excitation table of the circuit using the selected flip-flops.
  4. Obtain k-maps for each flip-flop input.
  5. Simplify the k-maps to obtain Boolean expressions for each flip-flop input.
  6. Draw the logic diagram of the circuit (if required).
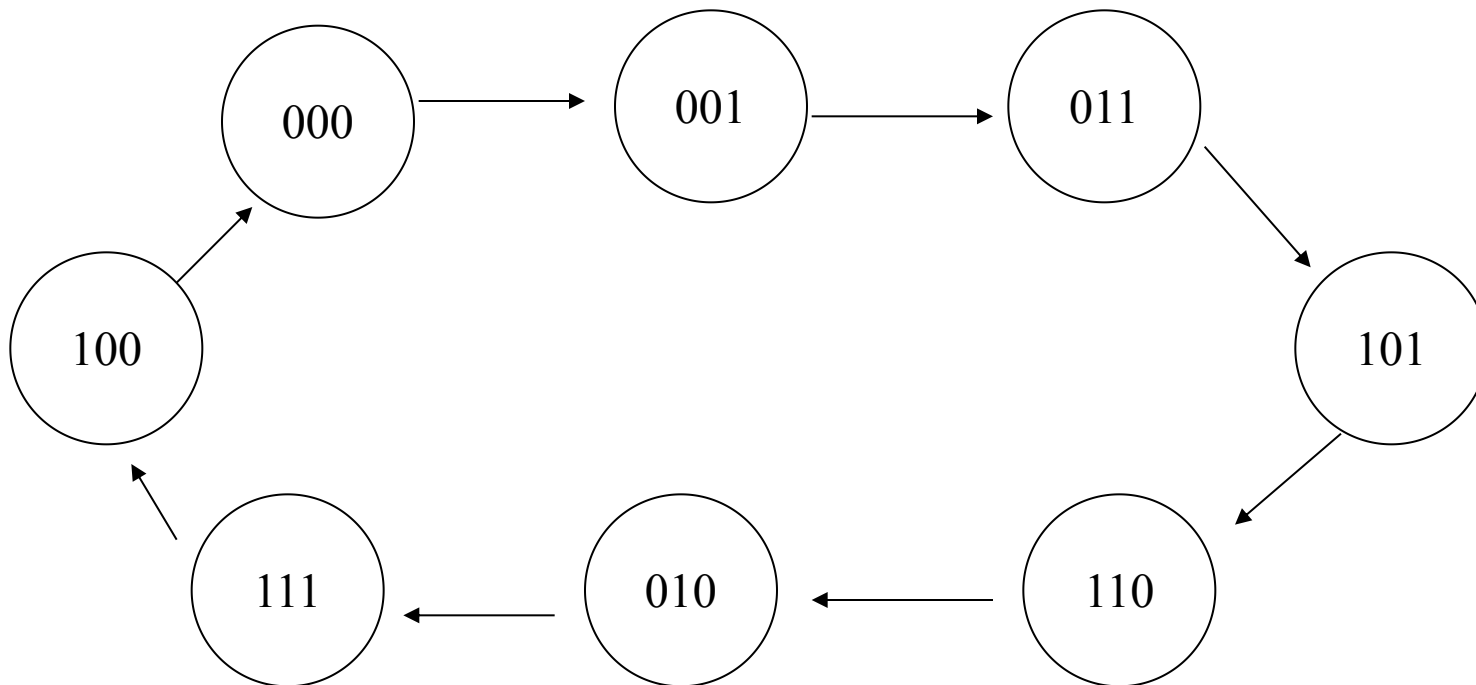
# Example

- Design a sequential circuit going through the following sequence of states: 0 -> 1 -> 3 -> 5 -> 6 -> 2 -> 7 -> 4 -> 0



(a) Draw the state diagram of the circuit.

# Excitation Table

---

Present state A B C			Next State A B C			flip-flop inputs T <sub>A</sub> T <sub>B</sub> T <sub>C</sub>		
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	1	1	1	1	0	1
0	1	1	1	0	1	1	1	0
1	0	0	0	0	0	1	0	0
1	0	1	1	1	0	0	1	1
1	1	0	0	1	0	1	0	0
1	1	1	1	0	0	0	1	1

# K-Map

$T_A$

AB

C

	00	01	11	10
0	0	1	1	1
1	0	1	0	0

$$T_A = A'B + AC'$$

$T_B$

AB

C

	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$T_B = C$$

$T_C$

AB

C

	00	01	11	10
0	1	1	0	0
1	0	0	1	1


$$T_C = A'C' + AC$$

Present state			Next State			flip-flop inputs		
A	B	C	A	B	C	$T_A$	$T_B$	$T_C$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	1	1	1	1	0	1
0	1	1	1	0	1	1	1	0
1	0	0	0	0	0	1	0	0
1	0	1	1	1	0	0	1	1
1	1	0	0	1	0	1	0	0
1	1	1	1	0	0	0	1	1

# More examples of sequential circuit synthesis.


- Design a two bit sequential circuit with an external input  $x$ , such that the circuit counts up when  $x=0$  and counts down when  $x=1$ . Use D flip-flops.

- a) Draw state diagram

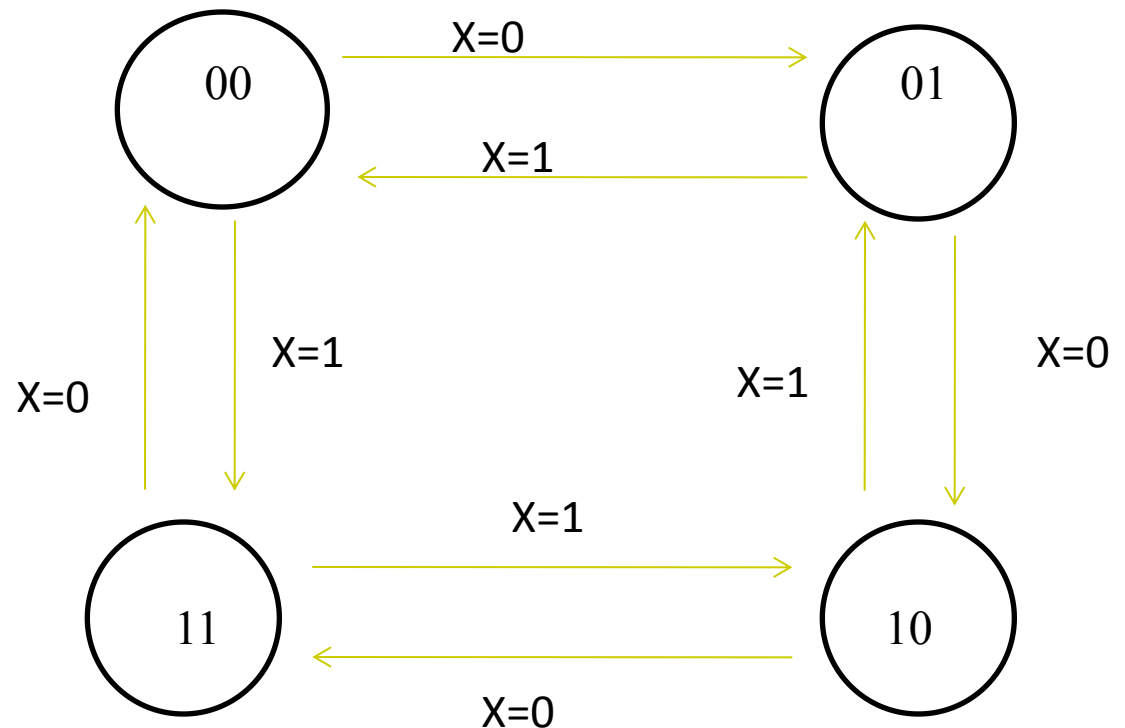

# Excitation Table

Present state			Next State		flip-flop Inputs	
A	B	x	A	B	DA	DB
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0

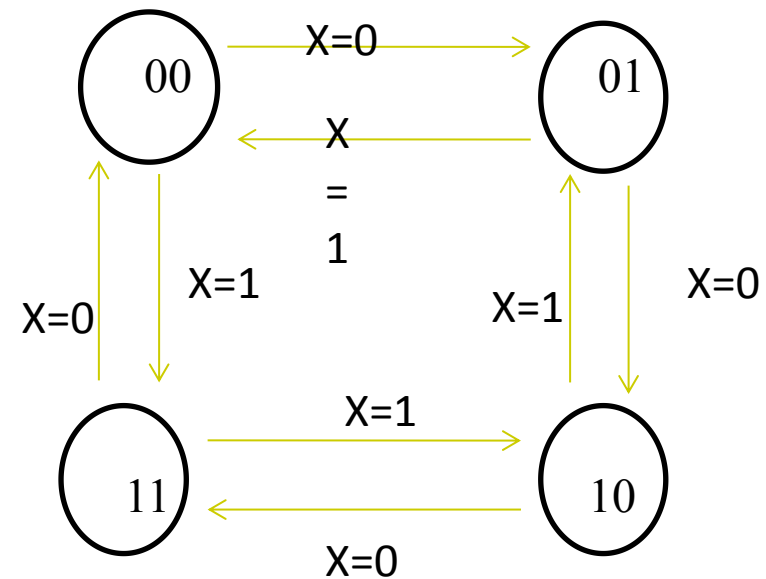

# K-maps

DA x	AB			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$DA = A'B'x + A'Bx' + AB'x' + ABx$$

DB x	AB			
	00	01	11	10
0	1	0	0	1
1	1	0	0	1


$$DB = B'$$

Present state			Next State		flip-flop Inputs	
A	B	x	A	B	DA	DB
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0




Draw the logic diagram.

---

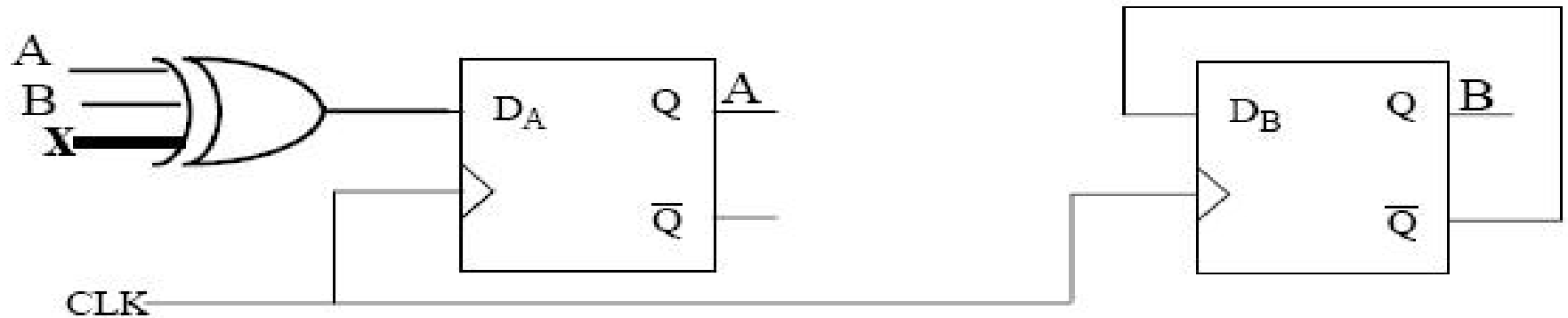


2. Design a sequential circuit, using T flip-flops, that has the following state diagram

---

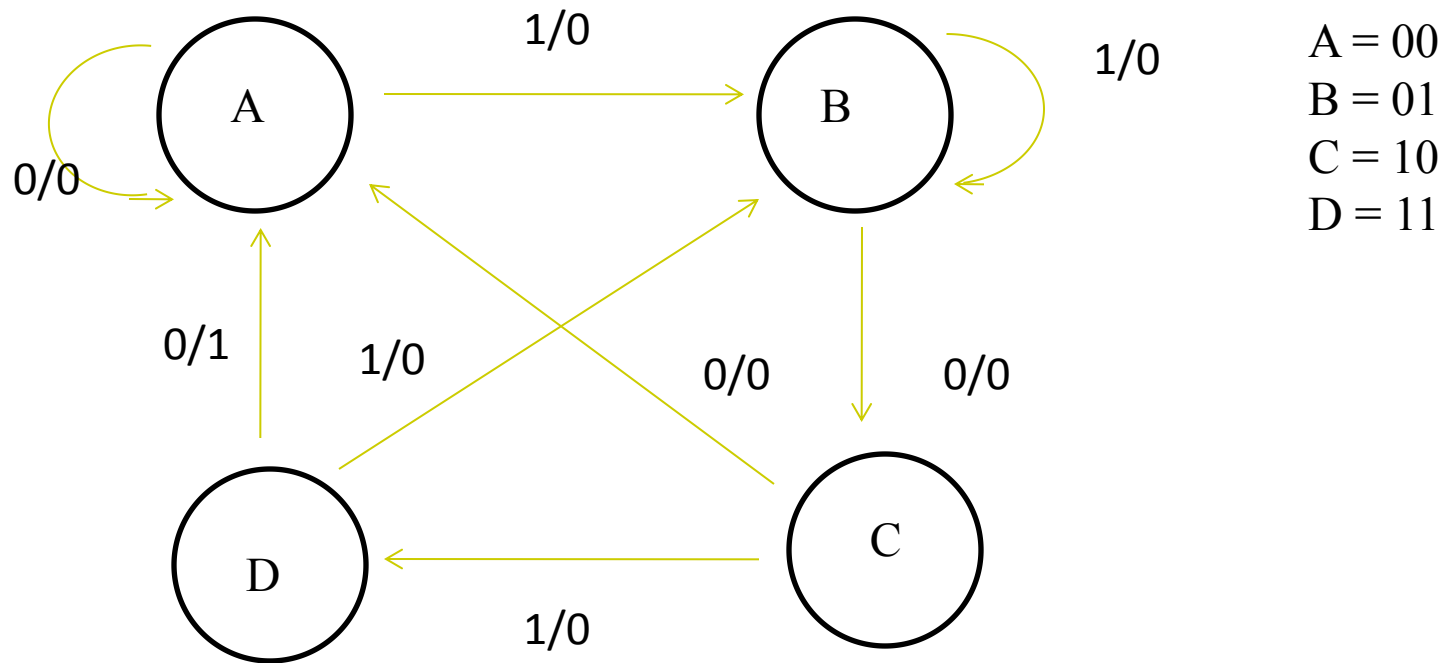

Fill in the excitation table corresponding to the above sequential circuit, using T flip-flops.

Present State			Next State		flip-flop Inputs		Output
Q1	Q2	X	Q1	Q2	T1	T2	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	1	0
0	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	1
1	1	1	0	1	1	0	0

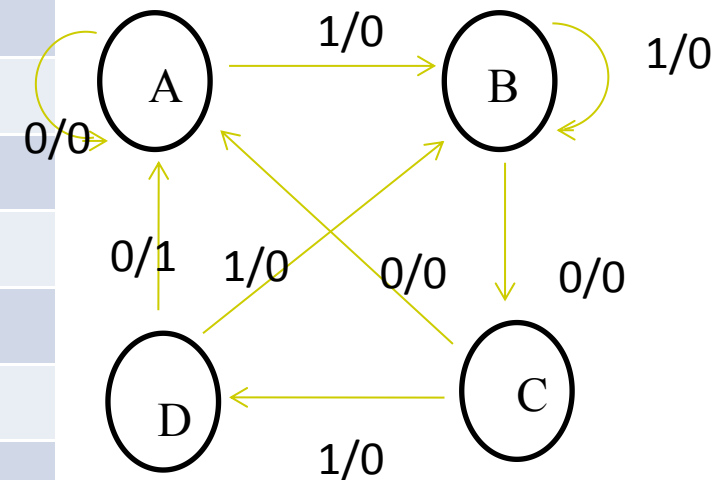

Fill in the K-maps and obtain a Boolean expression for each flip-flop input.

K-map for T1:

		Q1Q2			
		00	01	11	10
x	0	0	1	1	1
	1	0	0	1	0

$$T1 = Q1Q2 + Q1x' + Q2x'$$

K-map for T2:


		Q1Q2			
		00	01	11	10
x	0	0	1	1	0
	1	1	0	0	1

$$T2 = Q2x' + Q2'x$$

Present State			Next State		flip-flop Inputs		Output
Q1	Q2	X	Q1	Q2	T1	T2	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	1	0
0	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	1
1	1	1	0	1	1	0	0

Draw the logic diagram.


---

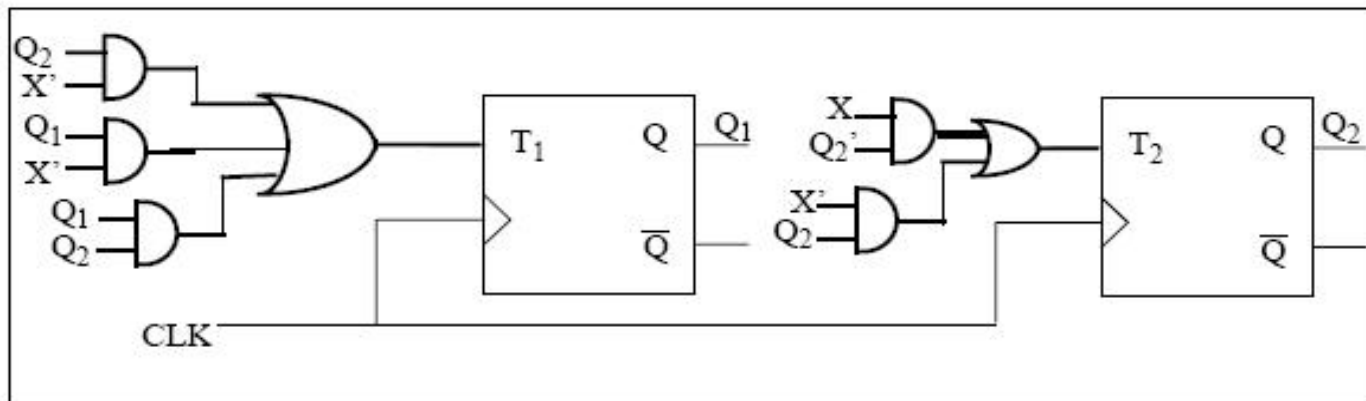
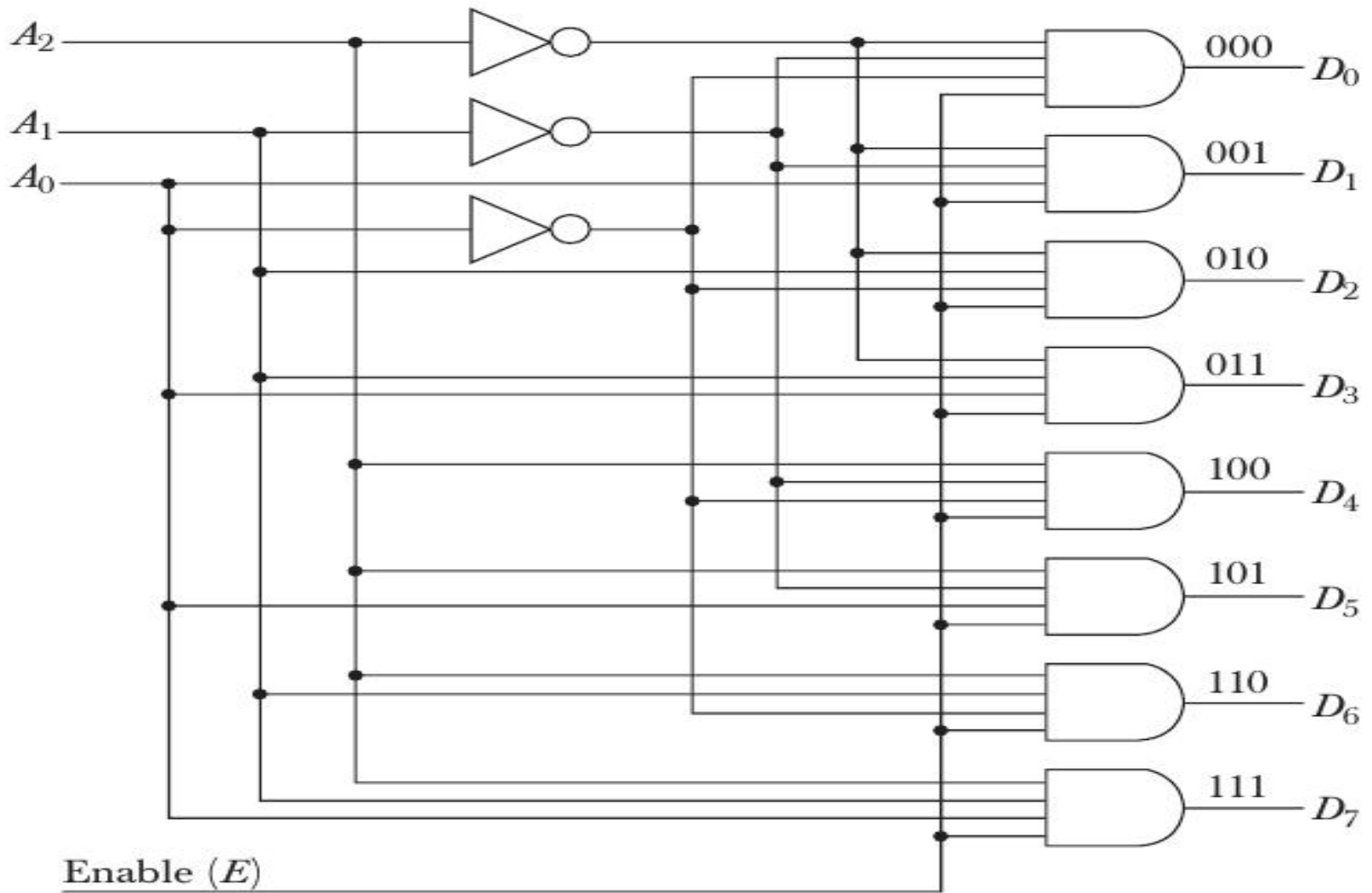
# Decoder

---

- ❑ Converts binary information from  $n$  inputs to upto  $2^n$  outputs.
- ❑ If some input combinations are unused, the number of outputs may be less.
- ❑ For each input combination, only one output is *active* and all other outputs are *inactive*.
- ❑ The decoders presented here are called n-to-m-line decoders, where  $m \leq 2^n$ .




**A decoder may also have an enable input ( $E$ ), as shown above.**


TABLE 2-1 Truth Table for 3-to-8-Line Decoder

Enable	Inputs			Outputs							
$E$	$A_2$	$A_1$	$A_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	×	×	×	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	0	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0



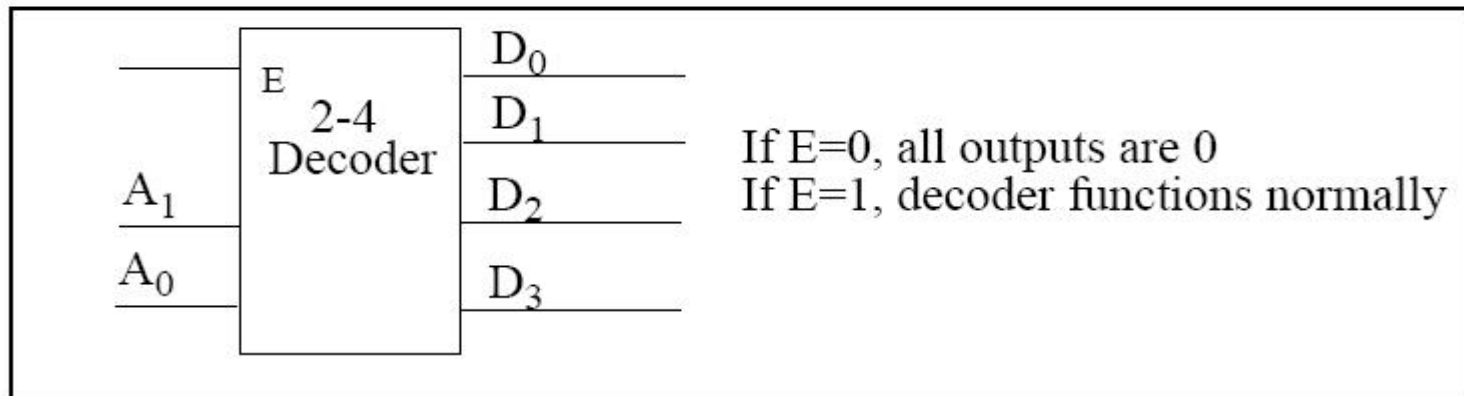

**Figure 2-3** 2-to-4-line decoder with NAND gates.

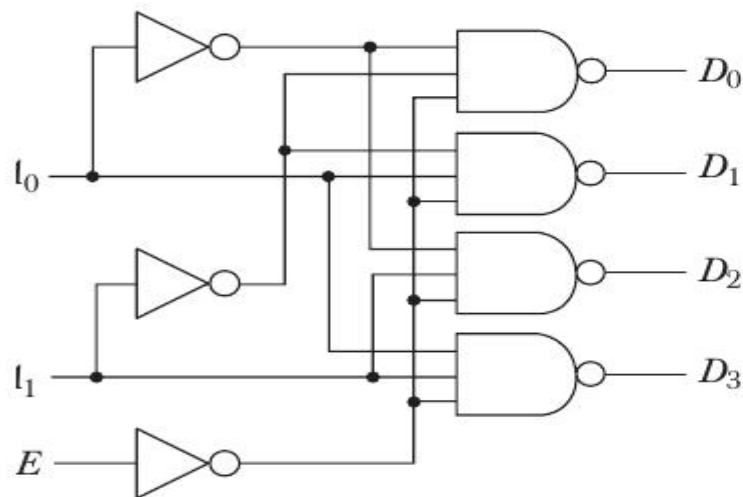


(a) Logic diagram

$E$	$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

(b) Truth table
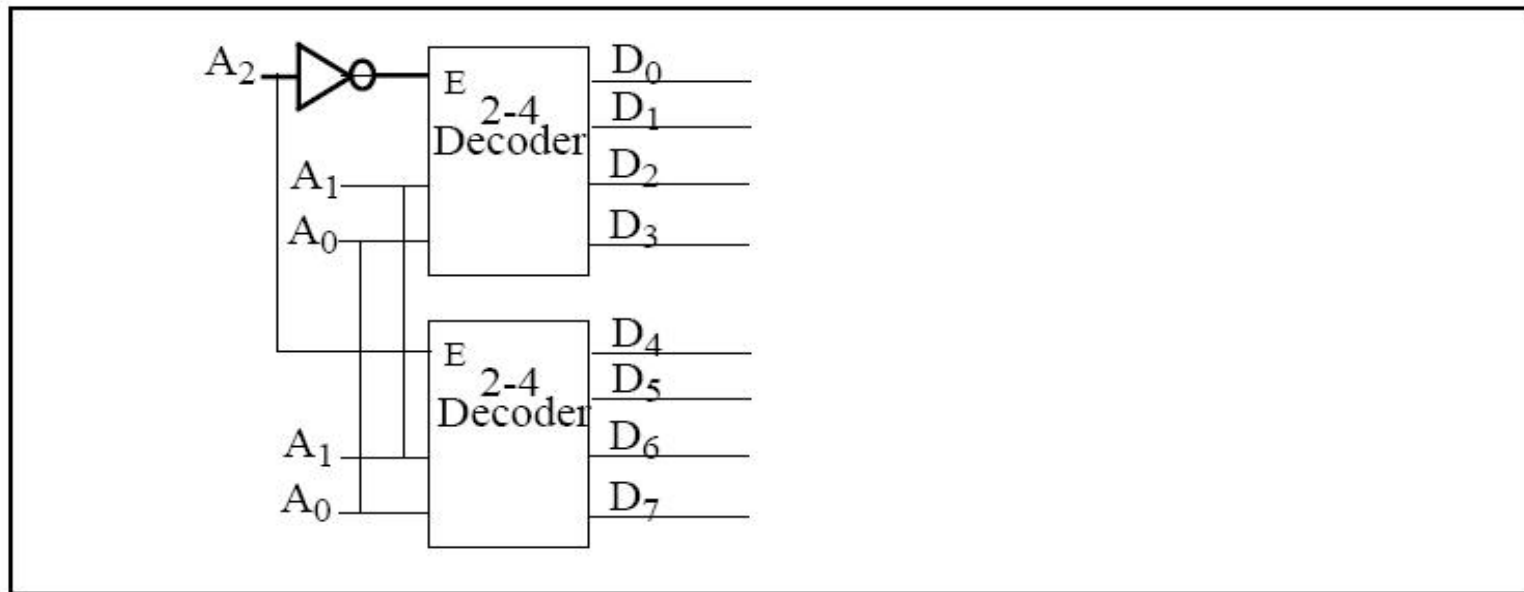
# Decoder Expansion:

- ❑ Smaller decoders can be combined to form a larger one.
- ❑ Example: Construct a 3-8 decoder using 2-4 decoders.



# Encoders

---

- ❑ An encoder performs the inverse operation of a decoder.
- ❑ It has (up to)  $2^n$  inputs and  $n$  outputs.
- ❑ The output lines generate the binary code corresponding to the input value.
- ❑ Only one input line can be high at any given time.

TABLE 2-2 Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1



$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$
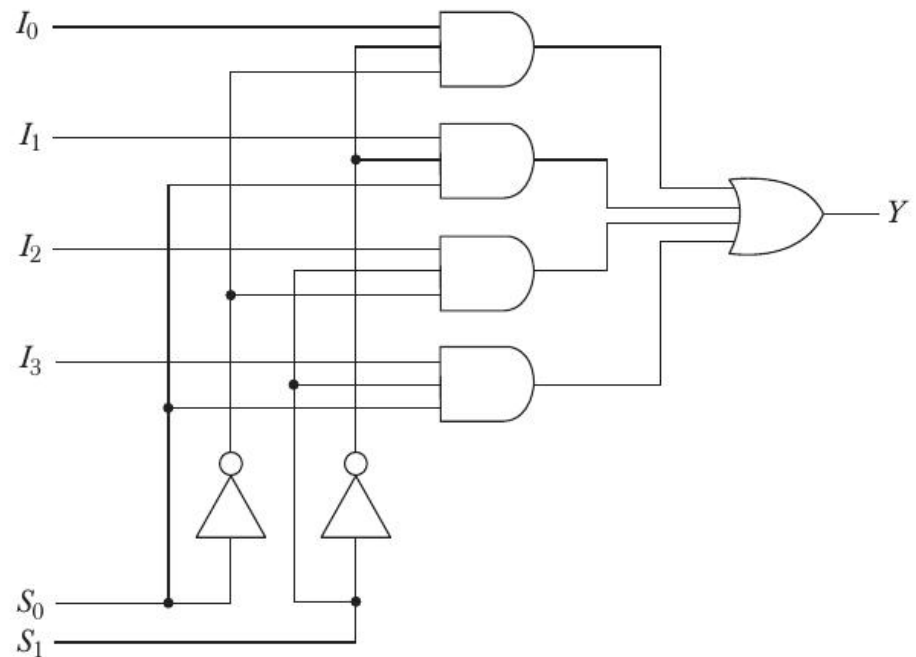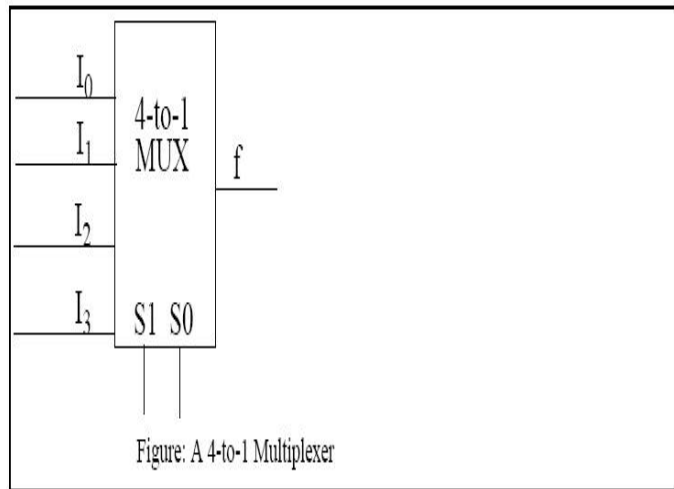
# Multiplexer

- ❑ A combinational circuit which takes information from one of  $2^n$  input lines and transfers it to a single output line.
- ❑ The particular input line chosen is determined by  $n$  select lines.




---

**TABLE 2-3** Function Table for 4-to-1-Line Multiplexer

Select		Output
$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$
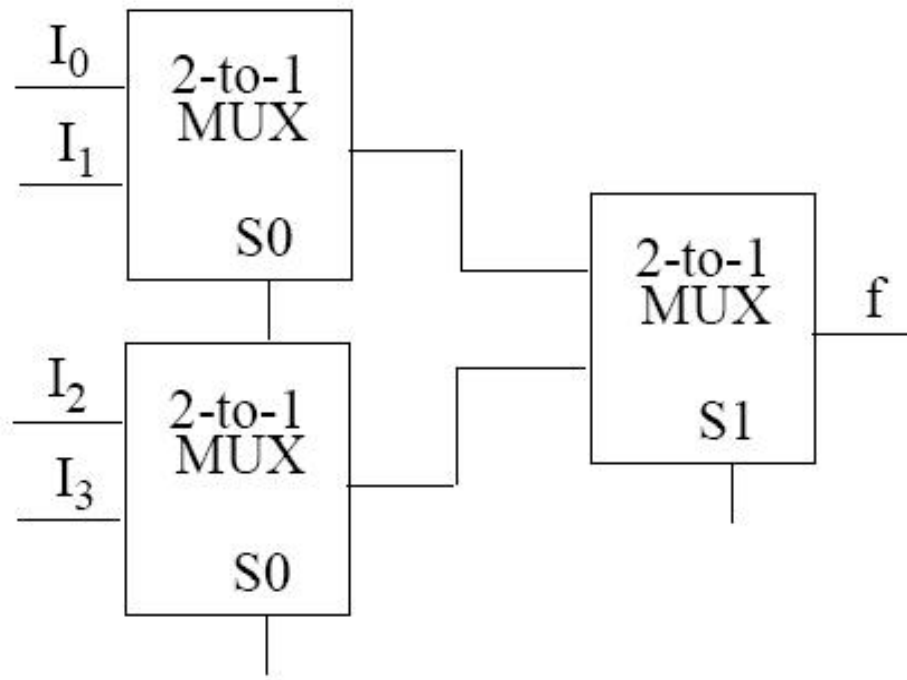
# Multiplexer Expansion

- Smaller multiplexers can be combined to form a larger one.
- Example: Construct a 4-to-1 multiplexer using 2-to-1 multiplexers.



# Registers


---


- ❑ A group of flip-flops, where each flip-flop stores 1 bit of information.
- ❑ A  $n$ -bit register consists of  $n$  flip-flops and can store any binary information of  $n$  bits.
- ❑ May have combinational circuits associated with each flip-flop, for simple data processing operations such as LOAD, INR, INV etc.
- ❑ The flip-flops hold binary information and the combinational circuits control how and when new information is transferred to the register.


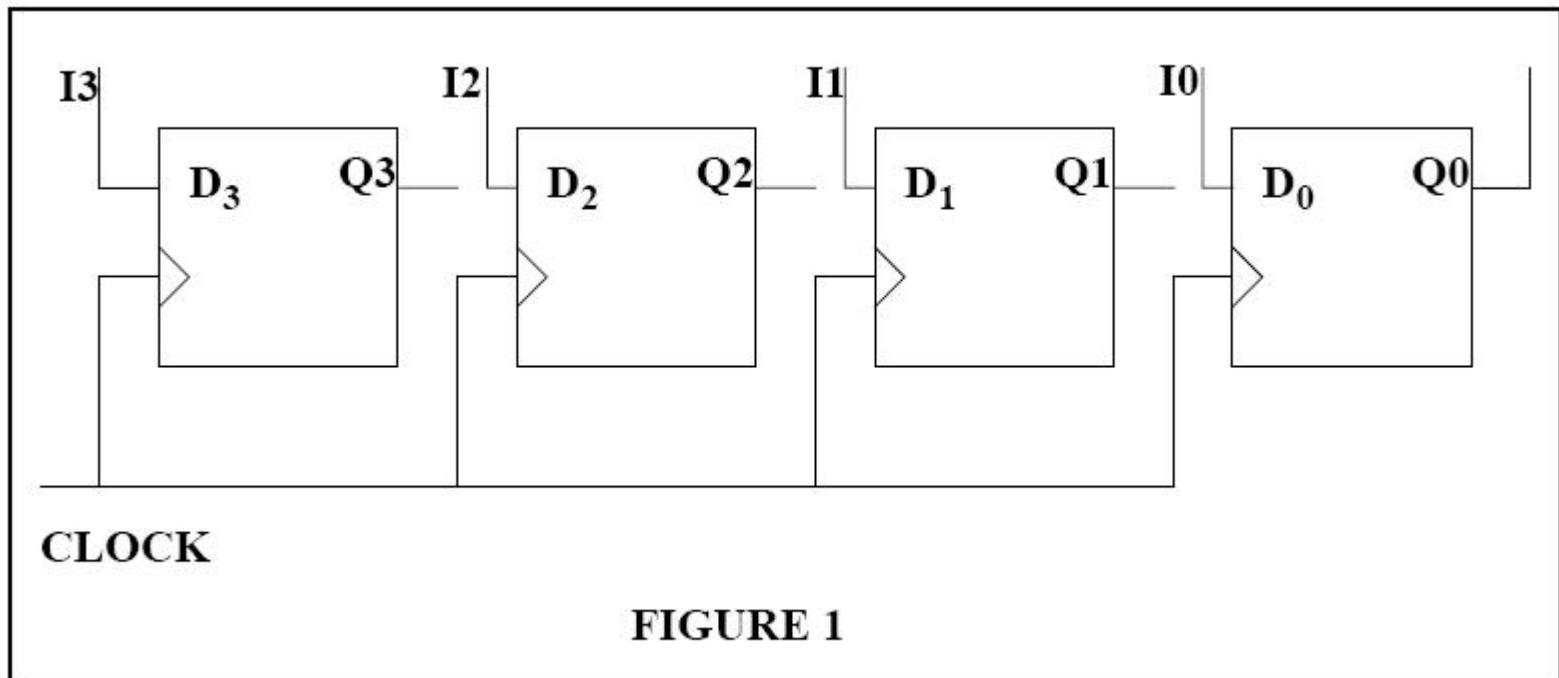
# Registers

- Figure 1 shows a simple 4-bit register with parallel load. A positive clock transition will load all 4 values I3 - I0 into the register.



 - 
- 
- ❑ In a digital system a clock generator supplies a continuous set of clock pulses.
  - ❑ A separate control signal (LOAD) is required to determine which clock pulse affects the data in a register.
  - ❑ When  $\text{LOAD} = 1$ , a new value is loaded into the register.
  - ❑ When  $\text{LOAD} = 0$ , the contents of the register remains unchanged.

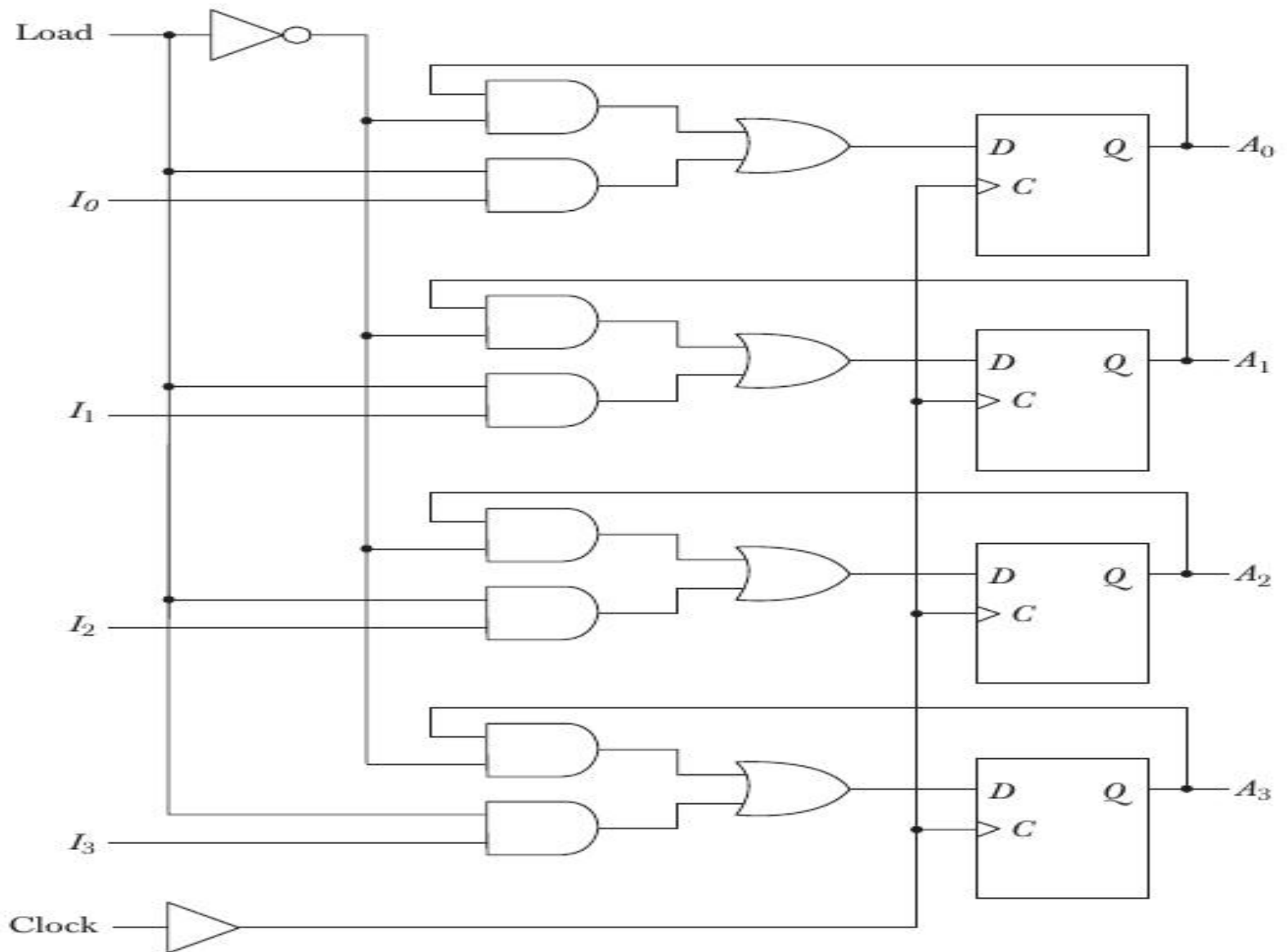


Figure 2-8 4-bit register with parallel load.


# Shift Registers

---

- ❑ A register capable of shifting binary information in one or both directions.
- ❑ It consists of a chain of flip-flops in cascade, with the output of one stage connected to the input of the next stage.
- ❑ All flip-flops receive a common clock pulse.
- ❑ A shift register that can shift in both directions is called a *bidirectional* shift register.

# Shift registers

---

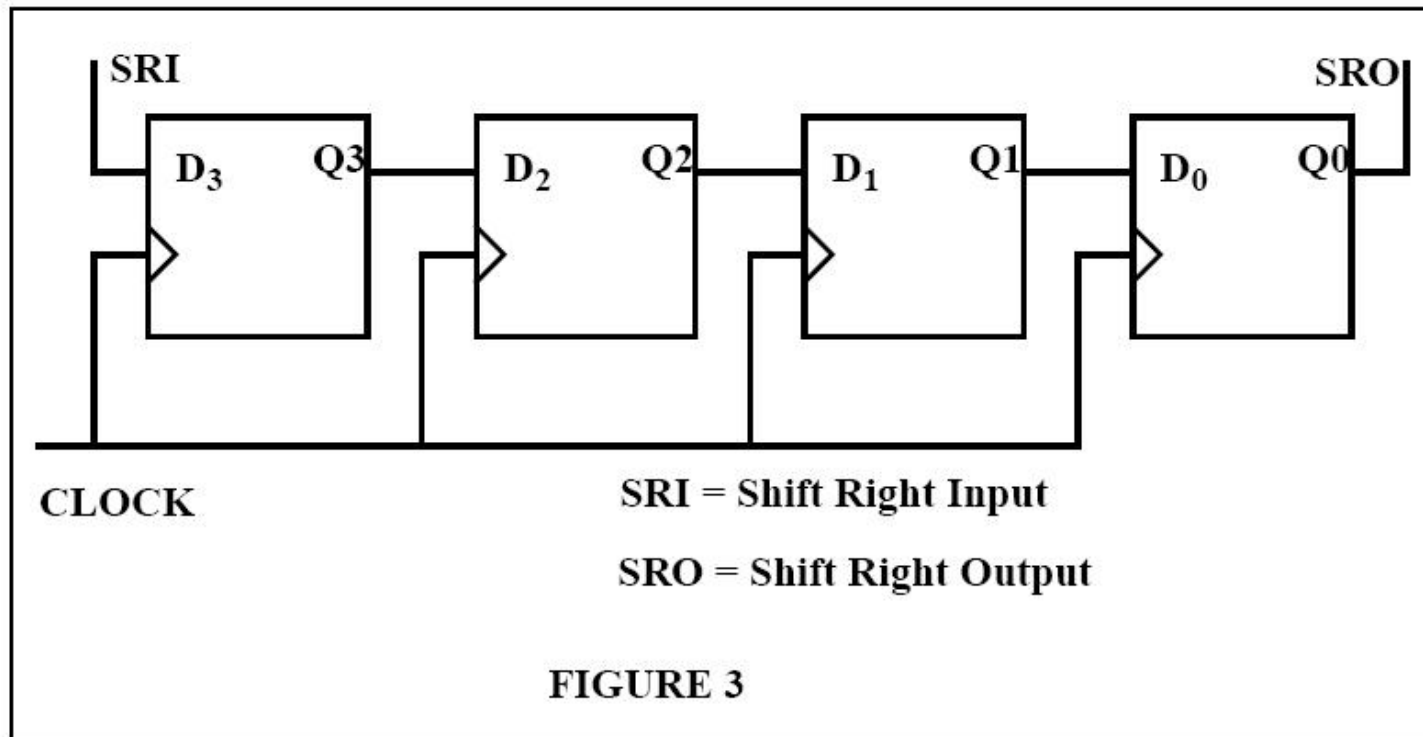

# Bidirectional Shift Registers with Parallel Load

---

- Unidirectional and Bidirectional Shift Registers
- The most general shift register has all the capabilities listed below. Others may have some of these capabilities, with at least one shift operation.
  - An input for clock pulses to synchronize all operations.
  - A shift-right operation and a serial input line associated with the shift-right.
  - A shift-left operation and a serial input line associated with the shift-left.
  - A parallel load operation and n input lines associated with the parallel transfer.
  - n parallel output lines.
  - A control state that leaves the information in the register unchanged even though clock pulses are applied continuously.

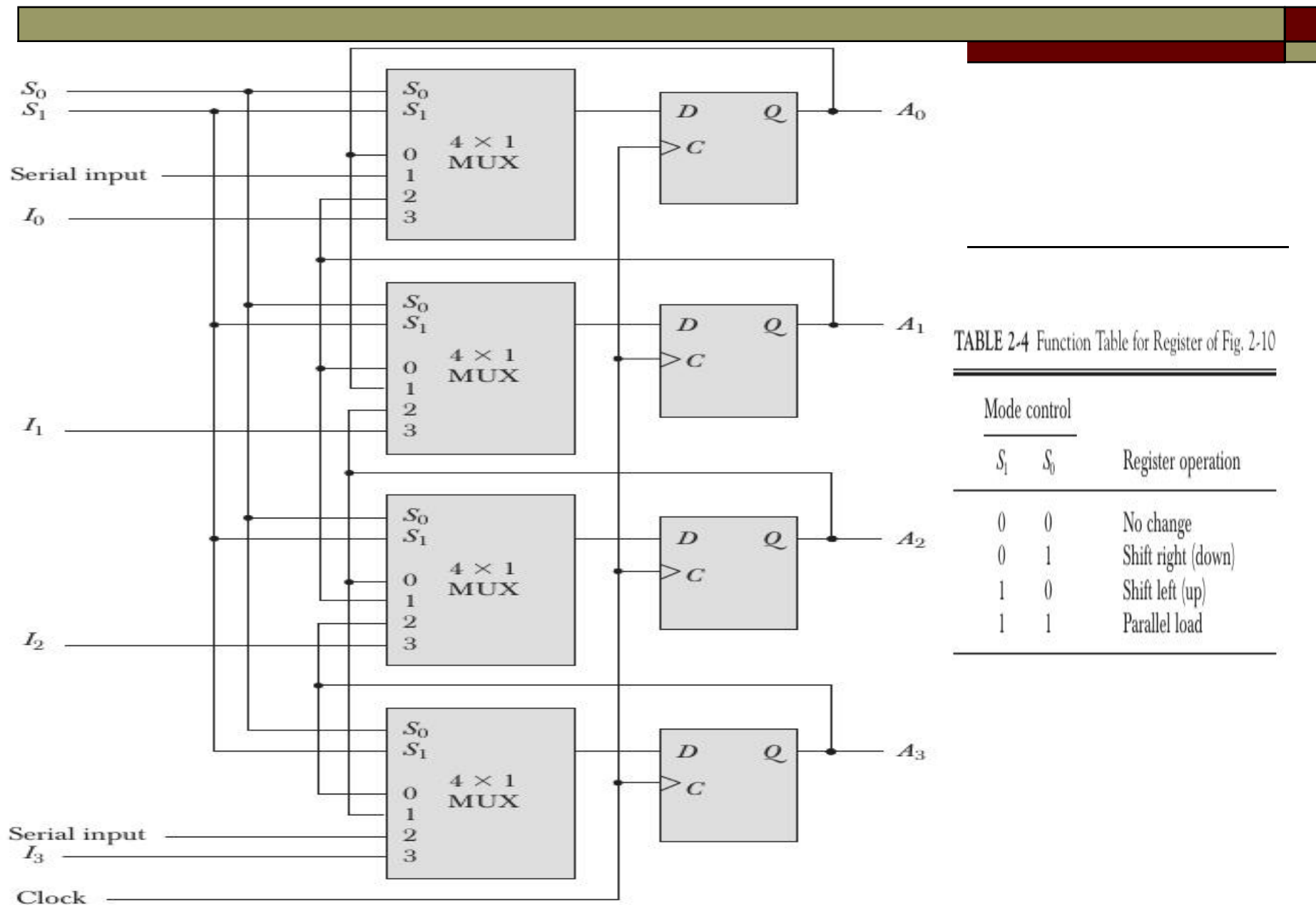


TABLE 2-4 Function Table for Register of Fig. 2-10

Mode control		Register operation
$S_1$	$S_0$	
0	0	No change
0	1	Shift right (down)
1	0	Shift left (up)
1	1	Parallel load

Figure 2-10 Bidirectional shift register with parallel load.

# Counters

---

- ❑ A register that goes through a prescribed sequence of states upon the application of input pulses is called a counter.
- ❑ The input pulses may be clock pulses, or they may originate from some external source and may occur at a fixed interval of time or at random.
- ❑ Sequence may be binary or any other sequence of states.
- ❑ A counter that follows the binary number sequence is called a binary counter. ( $n$ -bits  $\rightarrow 2^{n-1}$  combinations)





# Categorisation of Counters

---

## □ Ripple Counter


- A flip-flop output transition serves as a source for triggering other flip-flops.

## □ Synchronous Counter


- The C inputs of all flip-flops receive the common clock.
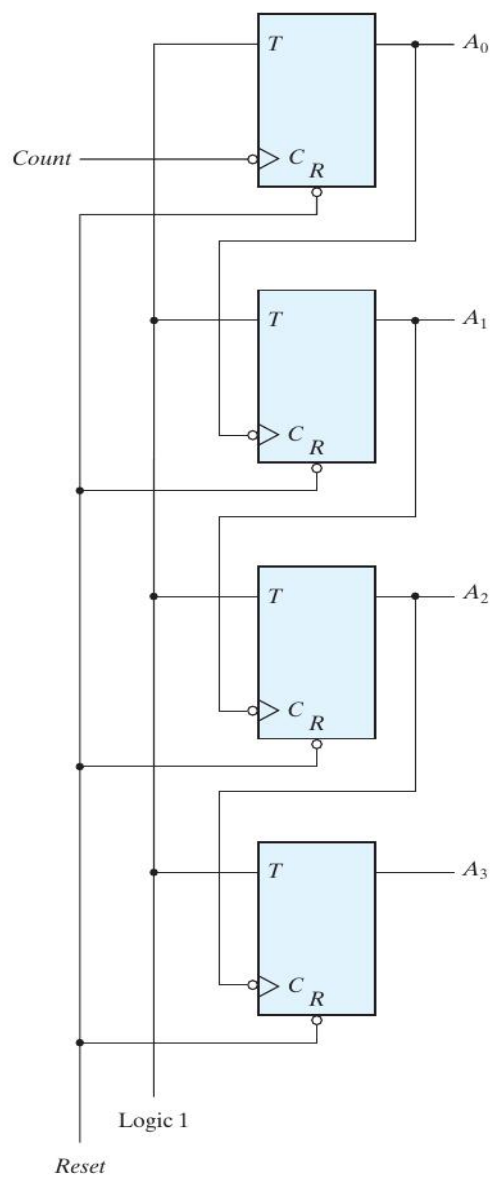
# Binary Ripple Counter

- 
- A binary ripple counter consists of a series connection of complementing flip-flops (either JK or T flip-flops), with the output of each flip-flop connected to the clock input of the next higher order flip-flop.
  - The flip-flop holding the least significant bit receives the incoming count pulses.
  - The small circle indicates that the flip-flop complements during a negative-going transition.



(a) With *T* flip-flops

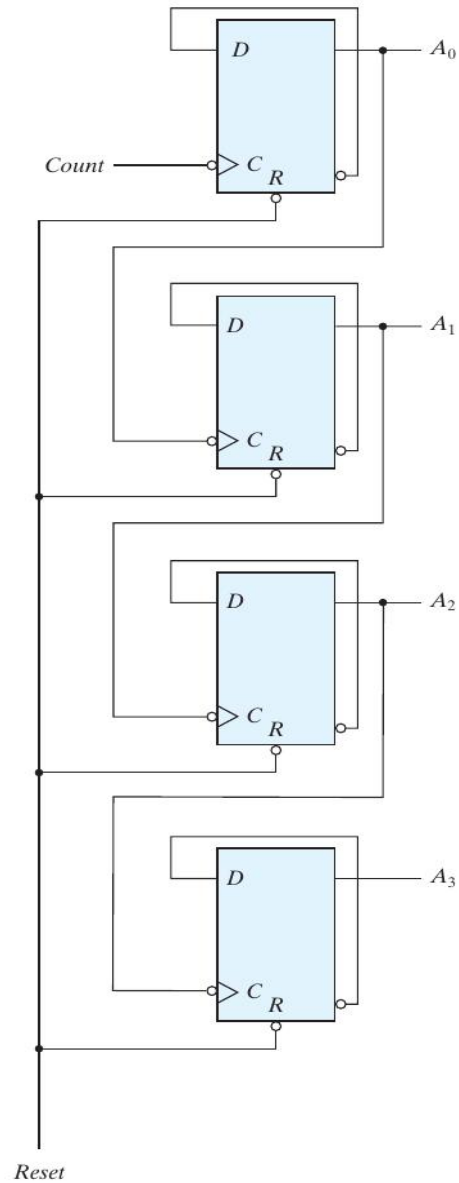

(b) With *D* flip-flops

### Count Sequence for a Binary Ripple Counter

Count Sequence					Conditions for Complementing Flip-Flops	
$A_4$	$A_3$	$A_2$	$A_1$		Complement $A_1$	$A_1$ will go from 1 to 0 and complement $A_2$
0	0	0	0		Complement $A_1$	$A_1$ will go from 1 to 0 and complement $A_2$ ;
0	0	0	1		Complement $A_1$	$A_2$ will go from 1 to 0 and complement $A_3$
0	0	1	0		Complement $A_1$	$A_1$ will go from 1 to 0 and complement $A_2$
0	0	1	1		Complement $A_1$	$A_1$ will go from 1 to 0 and complement $A_2$
0	1	0	0		Complement $A_1$	$A_1$ will go from 1 to 0 and complement $A_2$ ;
0	1	0	1		Complement $A_1$	$A_2$ will go from 1 to 0 and complement $A_3$ ;
0	1	1	0		Complement $A_1$	$A_3$ will go from 1 to 0 and complement $A_4$
0	1	1	1		Complement $A_1$	
1	0	0	0		and so on . . .	

# Binary Ripple Counter- countdown

---


- ❑ A binary counter with a reverse count is called a binary countdown counter. In a countdown counter, the binary count is decremented by 1 with every input count pulse.
- ❑ Can be implemented by taking the outputs from the complementary output terminals of all the output ffs.
- ❑ It can also be implemented by transiting the outputs when bit goes from 0 to 1.



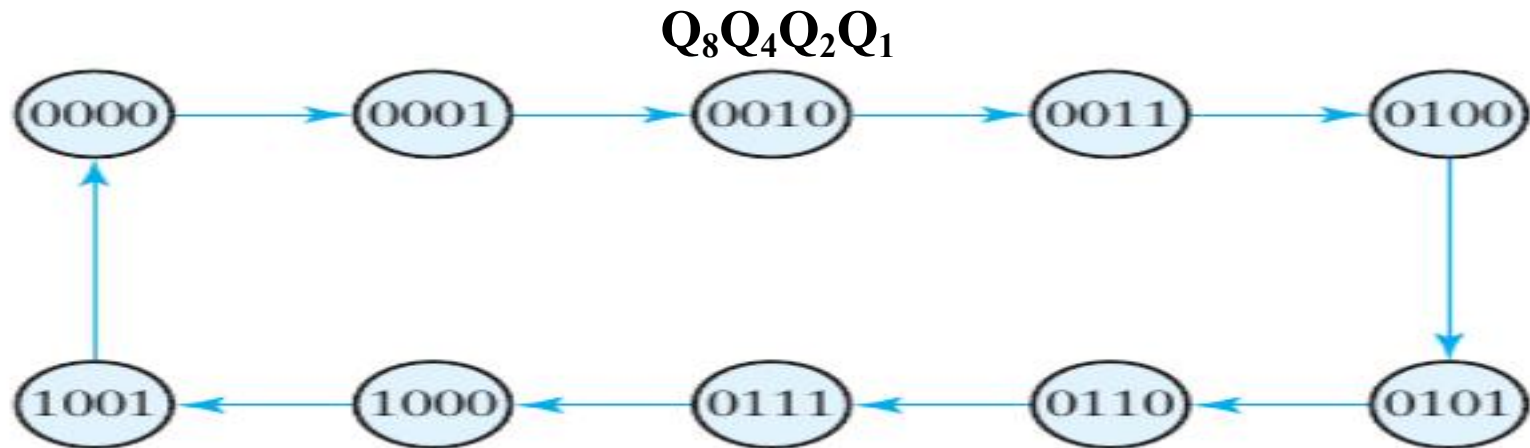
# BCD Ripple Counter

---

- A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9.
- A decimal counter is similar to a binary counter, except that the state after 1001 is 0000.




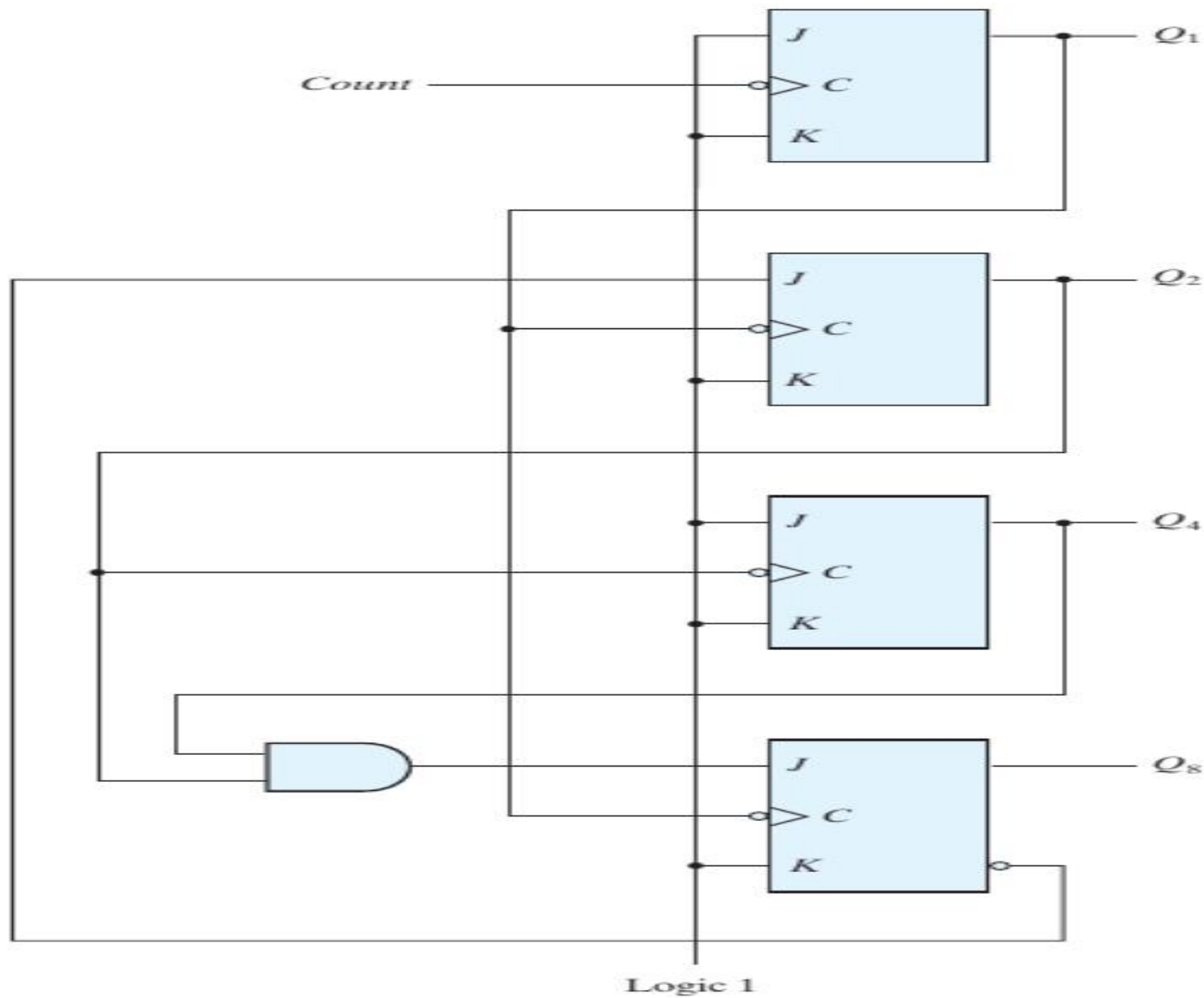1.  $Q_1$  is complemented on the negative edge of every count pulse.
2.  $Q_2$  is complemented if  $Q_8 = 0$  and  $Q_1$  goes from 1 to 0.  $Q_2$  is cleared if  $Q_8 = 1$  and  $Q_1$  goes from 1 to 0.
3.  $Q_4$  is complemented when  $Q_2$  goes from 1 to 0.
4.  $Q_8$  is complemented when  $Q_4 Q_2 = 11$  and  $Q_1$  goes from 1 to 0.  $Q_8$  is cleared if either  $Q_4$  or  $Q_2$  is 0 and  $Q_1$  goes from 1 to 0.



# Multiple Decade Counter

---

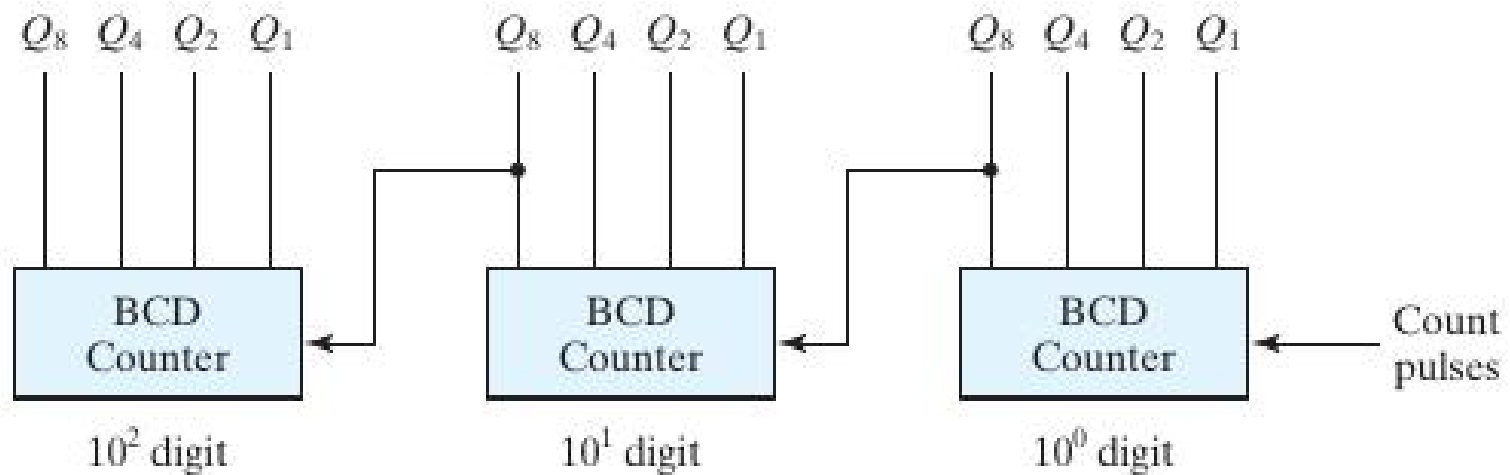



# Synchronous Counter

---

- Clock pulses are applied to all the flip-flops simultaneously.
- The decision whether a flip-flop is to be complemented or not is determined from the values of J and K inputs at the time of pulse.



---

## □ **Binary Counter:**



- The flip-flop in the lowest-order position is complemented with every pulse.
- A flip-flop in any other position is complemented with a pulse provided all the bits in the lower-order positions are equal to 1.
  - e.g. 0011 --> 0100

## □ **Binary Count-Down Counter:**

- The flip-flop in the lowest order position is complemented with every pulse.
- A flip-flop in any other position is complemented with a pulse provided all the lower-order bits are equal to 0.
  - e.g. 1100 --> 1011

# Excitation Table for 3-Bit Counter

Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

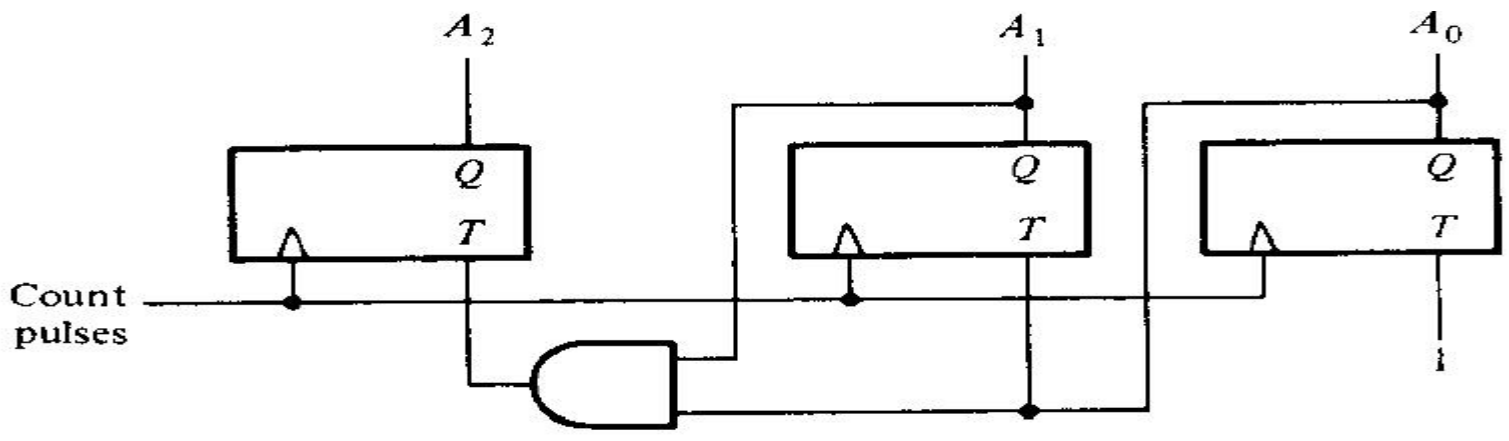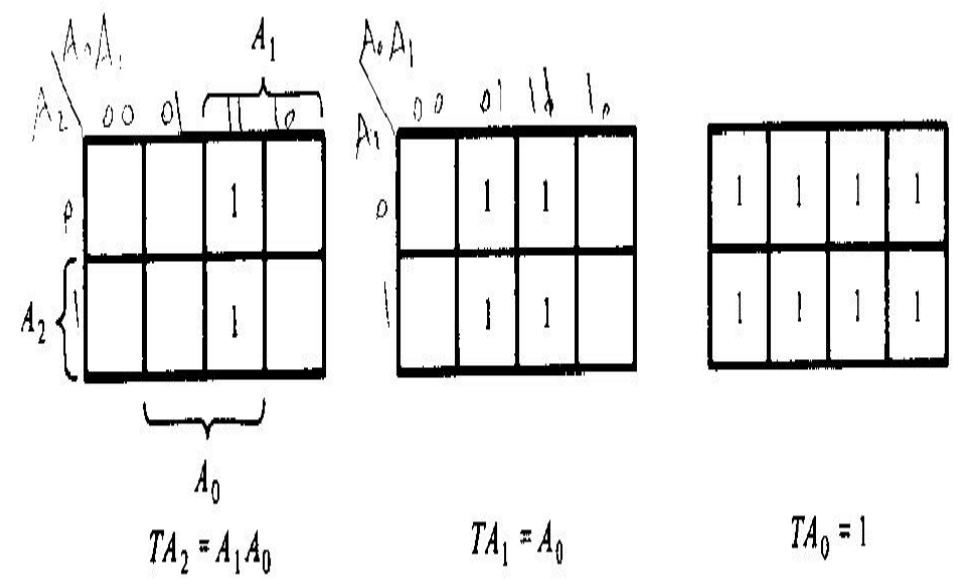

# BCD Counter

---

$$TQ_1 = 1$$

$$TQ_2 = Q_8' Q_1$$

$$TQ_4 = Q_2 Q_1$$

$$TQ_8 = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1$$

# Capacity of Memory

---

- ❑ Total number of bytes that can be stored in the memory.
- ❑ Capacity = no. of words x no. of bytes per word.
- ❑ Address lines are used to select one particular word in memory.
- ❑ A memory with  $2^k$  locations requires  $k$  address lines.

# Examples

---

(i) How many address and data lines\* are needed for a 64K x 8 bit memory.

$$64K = 2^6 \times 2^{10} = 2^{16}.$$

So, 16 address lines are needed.

wordlength = 8 bits. So, 8 data lines are needed.

(ii) How many address and data lines are needed for a 16M x 4 byte memory.

$$16M = 2^4 \times 2^{20} = 2^{24}.$$

So, 24 address lines are needed.

wordlength = 4 bytes = 32 bits. So, 32 data lines are needed

\*Assume the entire word is accessed as a unit.



# Random Access Memory (RAM)

---

- ❑ Memory cells from any location can be accessed directly.
- ❑ Process of locating a word in memory is the same and takes the same amount of time for each location.
- ❑ RAM is capable of both READ and WRITE operations.

# Steps for accessing a memory location in a RAM

---

- ❑ 1) Apply address to address lines
- ❑ 2) Apply data bits to input data lines (for WRITE operation only)
- ❑ 3) Activate READ/WRITE control line
- ❑ 4) Read data from data output lines (for READ operation only)